



A WIDE-FREQUENCY-RANGE BRIDGE OSCILLATOR

Also
IN THIS ISSUE

	<i>Page</i>
TOROIDAL, DUST-CORE STANDARD INDUC- TORS	5
MISCELLANY	8

● **BRIDGE MEASUREMENTS**, antenna measurements, and many laboratory procedures require a stable, variable-frequency source of moderate power output. The standard-signal generator, while adequate for most purposes, is not an economical solution because its output is low and because it includes amplifiers, meters, attenuators, etc., which are essential to its proper


function but are needless components in a laboratory signal source.

The TYPE 1330-A Bridge Oscillator was designed to provide a more satisfactory solution both technically and economically. This new oscillator is recommended for use with General Radio bridges such as the TYPE 716-C Capacitance Bridge, the TYPES 916-A and 916-AL Radio-Frequency Bridges, and the TYPE 821-A Twin T.

RANGE AND OUTPUT

The TYPE 1330-A Bridge Oscillator supplies three audio frequencies (power line frequency, 400 cycles, and 1000 cycles) and a wide continu-

Figure 1. Panel view of the Type 1330-A Bridge Oscillator.

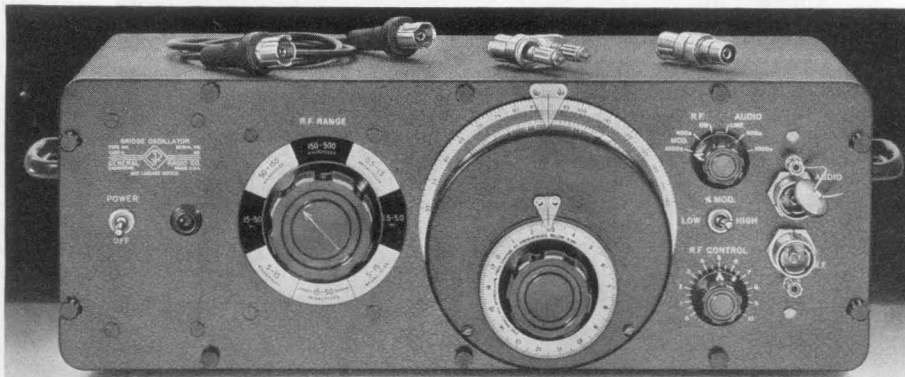

ous range of radio frequencies (5 kilocycles to 50 megacycles), either modulated or unmodulated.

The output voltage is of the order of ten volts. The output power into a 50-ohm load is more than one watt over most of the frequency spectrum. Typical output performance is indicated in Figure 4.


MOUNTING AND SHIELDING

In view of its rugged construction, wide-frequency range and appreciable power output, the new bridge oscillator is surprisingly compact. The relay-rack-type panel is only seven inches high. The aluminum cabinet is about nine inches deep and provides double shielding which reduces the stray field at one megacycle to about 50 microvolts per meter two feet from the instrument. The instrument can be easily removed from its cabinet and mounted in a relay-rack. Since the radio-frequency circuits are completely enclosed in a shielding compartment, the stray-field level is still sufficiently low for most applications.

TYPE 874 Coaxial Output Jacks are provided; the coaxial cable and adaptors supplied with the instrument permit complete shielding from the oscillator to the measuring instrument.

CONSTRUCTION

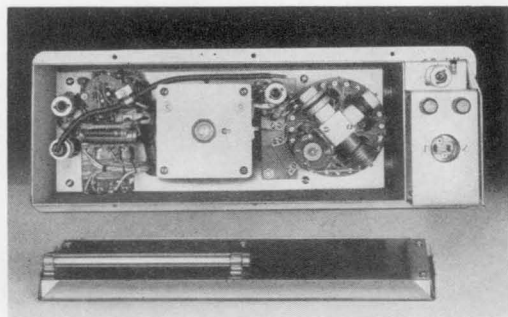Since frequency stability is very desirable in bridge measurements, the rugged mechanical construction used



in the TYPE 1001-A Standard-Signal Generator¹ was adopted for the new oscillator. The tuning capacitor has preloaded ball bearings mounted in 3/16-inch end plates and the end-plate supports are 1/2-inch diameter rods. The entire oscillator assembly is mounted on a 1/4-inch subpanel for complete rigidity. The radio-frequency range switch is taken bodily from the signal generator design to provide the eight coil turret positions. The r-f oscillator coils, however, are of different design, since the oscillator must deliver power directly to the load. For the same reason, the r-f oscillator tube is the higher-power type 6AQ5 miniature tube which has a rating of 12 watts plate dissipation.

The oscillator assembly plugs into a deep brass box and the double cover completes the shielding. Since the two leads entering the box are fully filtered and the four shafts extending from the box are enclosed in shielding sleeves, the leakage is at a minimum over the entire frequency range in spite of the high voltage level inside the box, necessitated by the power output requirements.

The power-supply, on a separate bracket, is mounted alongside the r-f compartment.

CIRCUIT

The radio-frequency oscillator is the Hartley type with its tapped coil and "floating" rotor and stator of the tuning capacitor. The higher-frequency components are quite conventional in design. At the lower radio frequencies, the plate and grid coils are mounted adjacent to each other to permit propor-

¹A. G. Bousquet, "General Purpose A-M Standard-Signal Generator," *General Radio Experimenter*, September, 1949.

Figure 2. Rear view with shield removed. Power supply unit is at the right of the assembly.

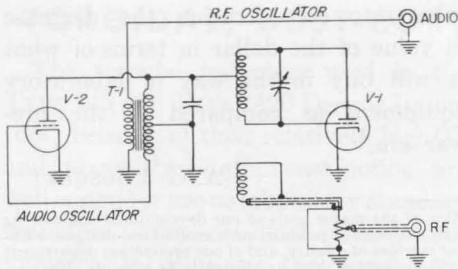


Figure 3. Elementary wiring diagram of Type 1330-A Bridge Oscillator.

tioning the coupling between the output coil and the plate and grid coils, for low carrier distortion.

Modulation of such a wide-frequency-range oscillator by the usual methods is not a simple matter. Since modulation is limited to two audio frequencies (400 and 1000 cycles), a novel and very effective method was devised for providing plate modulation. The plate-supply by-pass capacitor of the r-f oscillator is used as the tuning capacitor of the audio oscillator, thus dispensing with the modulating choke coils and r-f filters that inevitably cause dips in output at some frequency or other and upset the normal operating condition of the r-f oscillator. The method has resulted in excellent

modulation characteristics over the 15 kc to 50 Mc span. The shape of the tube characteristic is fortunately such as to compensate for any distortion in the audio oscillator. As a consequence, even though the audio oscillator distortion is about 5%, the envelope distortion of the modulated carrier is usually less than 5%, and at many points is less than 1%. The modulation level is either 30% or 60% as selected by the toggle switch on the panel.

COMPARISON

It is interesting to compare the new instrument with the prewar TYPE 684-A Modulated Oscillator² that for many years was the standard bridge oscillator. The new instrument is eleven pounds lighter, consumes only half as much power, and has about half the volume, yet it covers a wider frequency range, is more rugged, and supplies about ten times the output power at a much lower impedance level.

All of these improvements have been achieved at a lower real price, when we

²"A Radio-Frequency Source for the Laboratory," *General Radio Experimenter*, November, 1937.

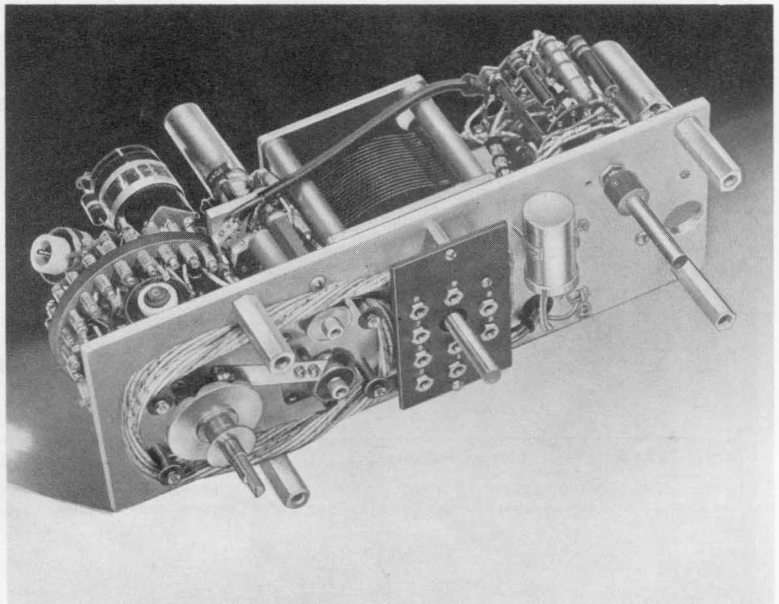


Figure 4. View of oscillator unit removed from cabinet. Servicing cable is shown coiled in its storage position.

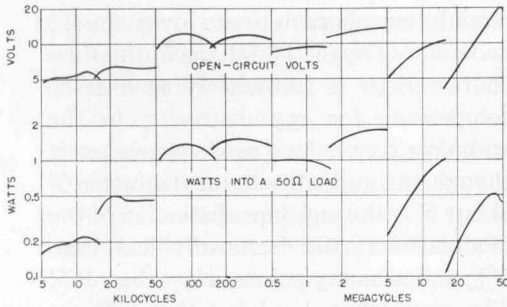


Figure 5. Output characteristics of the Type 1330-A Bridge Oscillator.

take into consideration the decrease in value of the dollar in terms of what it will buy in the way of laboratory equipment as compared to the pre-war era.³

—A. G. POUQUET

³One of the major goals of our development engineering staff has been to produce more economical designs, without sacrifice of quality, and of our production department to manufacture them as efficiently as possible. The success of this effort is attested to by the fact that General Radio prices have increased since 1939 by about 57%, as compared to an increase of over 84% in the general price index and over 100% in many other lines of durable goods.

SPECIFICATIONS

Frequency Range: Three fixed audio frequencies (power line frequency, 400 c, and 1000 c) and a continuous frequency spectrum from 5 kc to 50 Mc in eight direct-reading ranges as follows: 5 to 15 kc, 15 to 50 kc, 50 to 150 kc, 150 to 500 kc, 0.5 to 1.5 Mc, 1.5 to 5 Mc, 5 to 15 Mc, and 15 to 50 Mc.

Frequency Accuracy: $\pm 5\%$ for the 400- and 1000-cycle fixed frequencies, $\pm 2\%$ for the carrier frequencies above 150 kilocycles, and $\pm 3\%$ for the carrier frequencies below 150 kilocycles under no-load conditions. A 50-ohm resistive load may cause a frequency shift of as much as $+5\%$ at some of the lower carrier frequencies; above 150 kilocycles, the frequency shift due to a 50-ohm load is usually less than $+1\%$. From 5 kilocycles to 15 Mc, the dial calibration is logarithmic.

Incremental-Frequency Dial: The slow-motion dial indicates frequency increments of 0.1% per division from 5 kc to 15 Mc.

Output Voltage and Power: The AUDIO output jack provides a fixed voltage output of about 12 volts open circuit, or a power output of about $\frac{3}{4}$ watt into a matching 50-ohm load; the output at the R-F jack is controlled by the R-F control, and supplies adjustable output for the 5 kc to 50 Mc range; over the mid-frequency range, the open circuit output voltage is about ten volts and the output power into a 50-ohm load (output control at maximum) is about one watt. The output falls off at the upper and lower ends of the frequency spectrum.

Output Impedance: 50 ohms at the AUDIO jack; between 20 and 80 ohms, depending on frequency, at the R-F jack when the 300-ohm output control is at maximum.

Modulation: The R-F range (15 kc to 50 Mc) can be internally amplitude-modulated at either

400 c or 1000 c at the two modulation levels of approximately 30% and 60%. There is no provision for external modulation.

Envelope Distortion: Between 1% and 6% at the 60% modulation level.

R-F Distortion: 3% over most of the range; at the lower radio frequencies it is about 6%.

Leakage: Stray fields at 1 Mc are about 50 μ v per meter at two feet from the oscillator. With the instrument out of its cabinet, the stray field may be greater by a factor of ten.

Controls: A switch for selecting between AUDIO (LINE, 400 c, or 1000 c) and R-F output (CW or MODULATED — 400 c or 1000 c); a switch for selecting between HIGH and LOW modulation; a voltage divider for controlling the R-F output; a range switch; a calibrated dial and a vernier dial for setting the radio frequency; a power switch.

Accessories Supplied: TYPE 874-R21 3-foot Coaxial Cable, TYPE 874-Q2 Adaptor, TYPE 874-Q7 Adaptor, TYPE TO-44 Adjustment Tool, and a power cord.

Mounting: Aluminum panel finished in black-crackle lacquer. Aluminum cabinet is finished in black wrinkle and is provided with carrying handles. Cabinet can be removed for relay-rack mounting.

Power Supply: 115 (or 230) volts at 40 to 60 cycles. The power input is about 30 watts.

Tubes: Supplied with the instrument: Two 6AQ5-type tubes and one 6X4-type tube.

Terminals: TYPE 874 Coaxial Terminals are provided for both the AUDIO output and the R-F output.

Dimensions: (Height) 7 $\frac{1}{2}$ x (width) 21 $\frac{3}{4}$ x (depth) 11 $\frac{1}{4}$ inches overall.

Net Weight: 36 $\frac{1}{2}$ pounds.

Type	Code Word	Price
1330-A Bridge Oscillator.....	ACORN	\$525.00*

*U. S. Patent No. 2,125,816. Patent applied for. Licensed under patents of the Radio Corporation of America.